

CPSC 359 Final Exam Question 1

Name: Ayman Shahriar

UCID: 10180260

a) Determine the input and output variables, and assigning letter symbols to the variables:

There are three input variables:

- **z**: the “ones”
- **y**: the “twos”
- **x**: the “fours”

There are three output variables:

- **A**: the “ones”
- **B**: the “twos”
- **C**: the “fours”

b) Create a truth table

| x | y | z | A | B | C |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |

c) Find the simplified functions of each output using the map method:

Find the simplified function of A:

$$A = xy' + x'y$$

| | | y z | | | |
|---|---|-----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| x | 0 | 0 | 1 | 1 | 1 |
| | 1 | 1 | 1 | 0 | 0 |

Find the simplified function of B:

$$B = y'$$


| | | y z | | | |
|---|---|-----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| x | 0 | 1 | 1 | 0 | 0 |
| | 1 | 1 | 1 | 0 | 0 |

Find the simplified function of C :

$$C = Z$$

| | | | | | | | |
|---|---|----|---|----|----|----|----|
| | | y | | | | | |
| | | yz | | 00 | 01 | 11 | 10 |
| x | 0 | 0 | 1 | 3 | 2 | | |
| | 1 | 4 | 5 | 7 | 6 | | |
| | | z | | | | | |

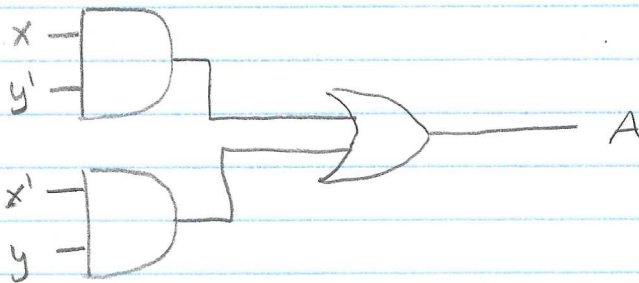d) Draw the logic diagram that implements the functions



y' ————— B

z ————— C

e) The design has been implemented in the Logisim file question1.circ