

Step 2: Create a state diagram

Note: Since the outputs of the counter are just the outputs of the flip-flops (ie. the counter outputs are the states of the flip-flops), the outputs are not explicitly shown in the arrows.

