

# CPSC 359 Assignment 1

Name: Ayman Shahriar


UCID: 10180260

## 1) Problem to solve:


We have to design a combinational logic circuit that takes a 4 bit number as input (from 0000 to 1111) and produce a unique 3x3 LED pattern as output.

Here are the following 16 display patterns corresponding to the input bit patterns

0000, 0001, 0010 ... 1111:

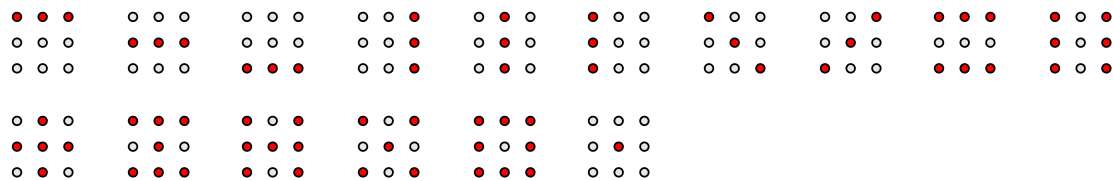

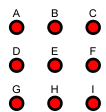The arrangement and labelling of the LED's are shown below:



## 2 & 3) Determining the input and output variables, and assigning letter symbols to the variables:

There are four input variables:

- **z**: the "ones"
- **y**: the "twos"
- **x**: the "fours"
- **w**: the "eights"

There are 9 output variables, each corresponding to an LED output:

- **A, B, C, D, E, F, G, H, I**

- 4) The truth table defining the relationship between the inputs and outputs is on page 3.
- 5) The simplified function for each output, as well as all the steps needed to obtain them, are in pages 4 - 6.
- 6) The logic diagrams for each output function are in pages 7 - 11.